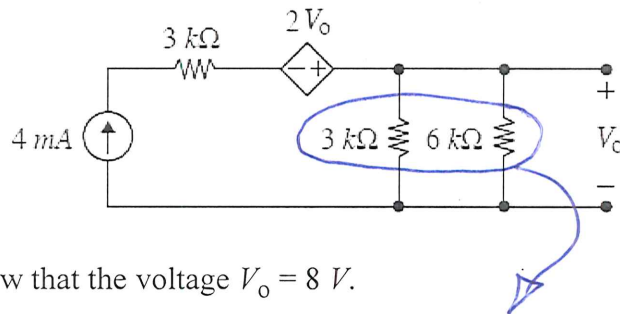


SA1 [5 Marks]. Consider the following circuit:



- (a) [2Marks] Show that the voltage $V_o = 8 \text{ V}$.

$$(3\text{k}\Omega) \parallel (6\text{k}\Omega) = \frac{(3\text{k}\Omega)(6\text{k}\Omega)}{(3\text{k}\Omega) + (6\text{k}\Omega)} = 2\text{k}\Omega$$

$$V_o = (4\text{mA})(2\text{k}\Omega) = 8\text{V}.$$

- (b) [3 Marks] Determine the amount of power absorbed or supplied by the dependent voltage source. Recall that a positive value indicates power absorbed.

4mA enters the neg. (low potential) side of the dep. voltage source \Rightarrow it is supplying energy/power.

$$\begin{aligned} P_{\text{abs}} &= (-2V_o)(4\text{mA}) \\ &= (-2)(8\text{V})(4\text{mA}) \\ &= -64\text{mW}. \end{aligned}$$