
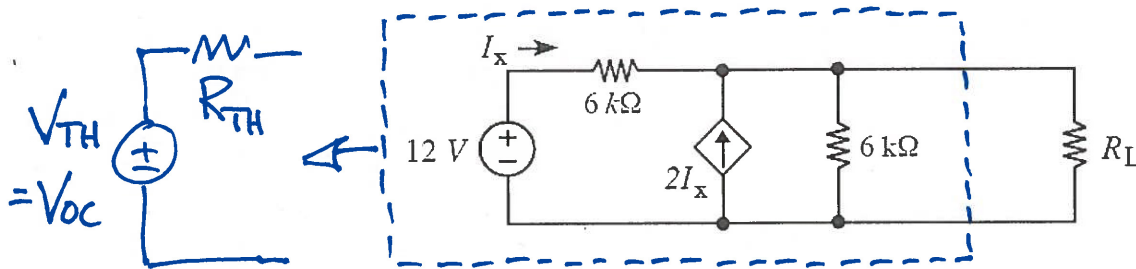


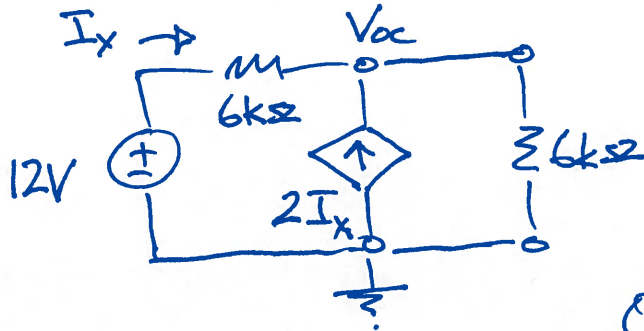SA 4. (5 marks) Consider the following circuit and determine the value of R_L that would result in the maximum amount of power transferred to it from the rest of the circuit. You do not need to calculate the value of the power.



The max. pwr. will be transferred if $R_L = R_{TH}$




$$\text{KCL: } -I_x - 2I_x + \frac{V_{OC}}{6k\Omega} = 0$$

$$-3I_x + \frac{V_{OC}}{6k\Omega} = 0 \quad \text{--- (1)}$$

$$\text{Ohm's Law: } I_x = \frac{12V - V_{OC}}{6k\Omega} \quad \text{--- (2)}$$

$$(2) \rightarrow (1): -3\left(2mA - \frac{V_{OC}}{6k\Omega}\right) + \frac{V_{OC}}{6k\Omega} = 0$$

$$\therefore V_{OC} = 9V$$

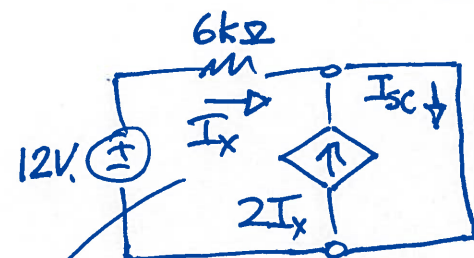


$$I_{SC} = I_x + 2I_x = 6mA$$

$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{9V}{6mA} = 1.5k\Omega$$


Here, $I_x = \frac{12V}{6k\Omega} = 2mA$

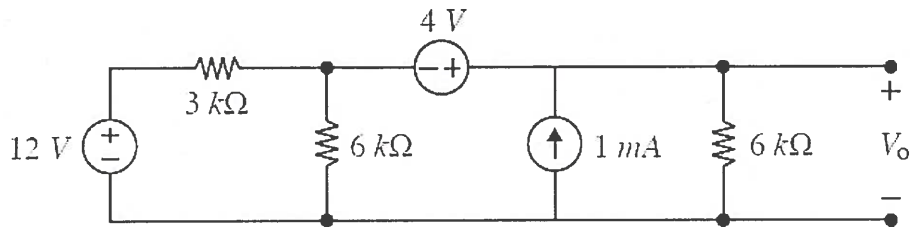Prob 2. (25 marks) Consider the following circuit that is to be analyzed using three different approaches:




(a) (7 marks) Use the Superposition Principle to determine the voltage V_0 .


(1) 4V source alone:

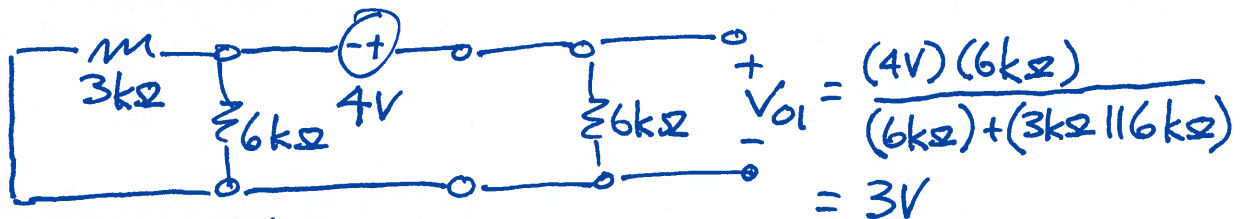

(2) 12V source alone:

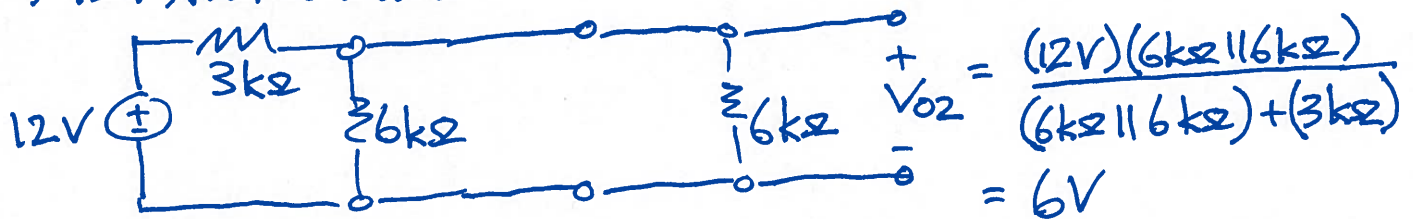


(3) 1mA source alone:

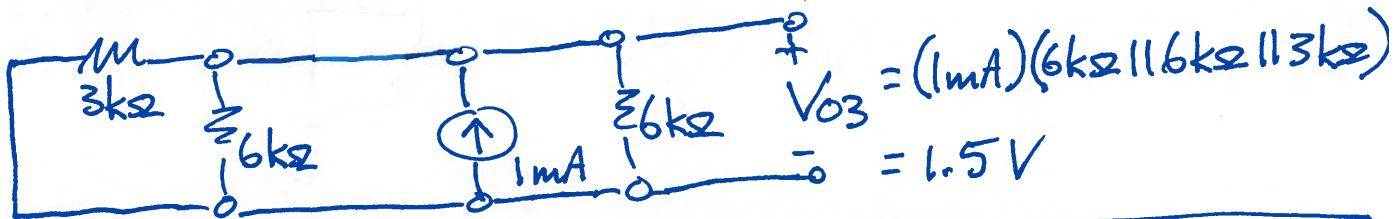


Superposition: $V_0 = V_{01} + V_{02} + V_{03} = 3V + 6V + 1.5V = 10.5V$

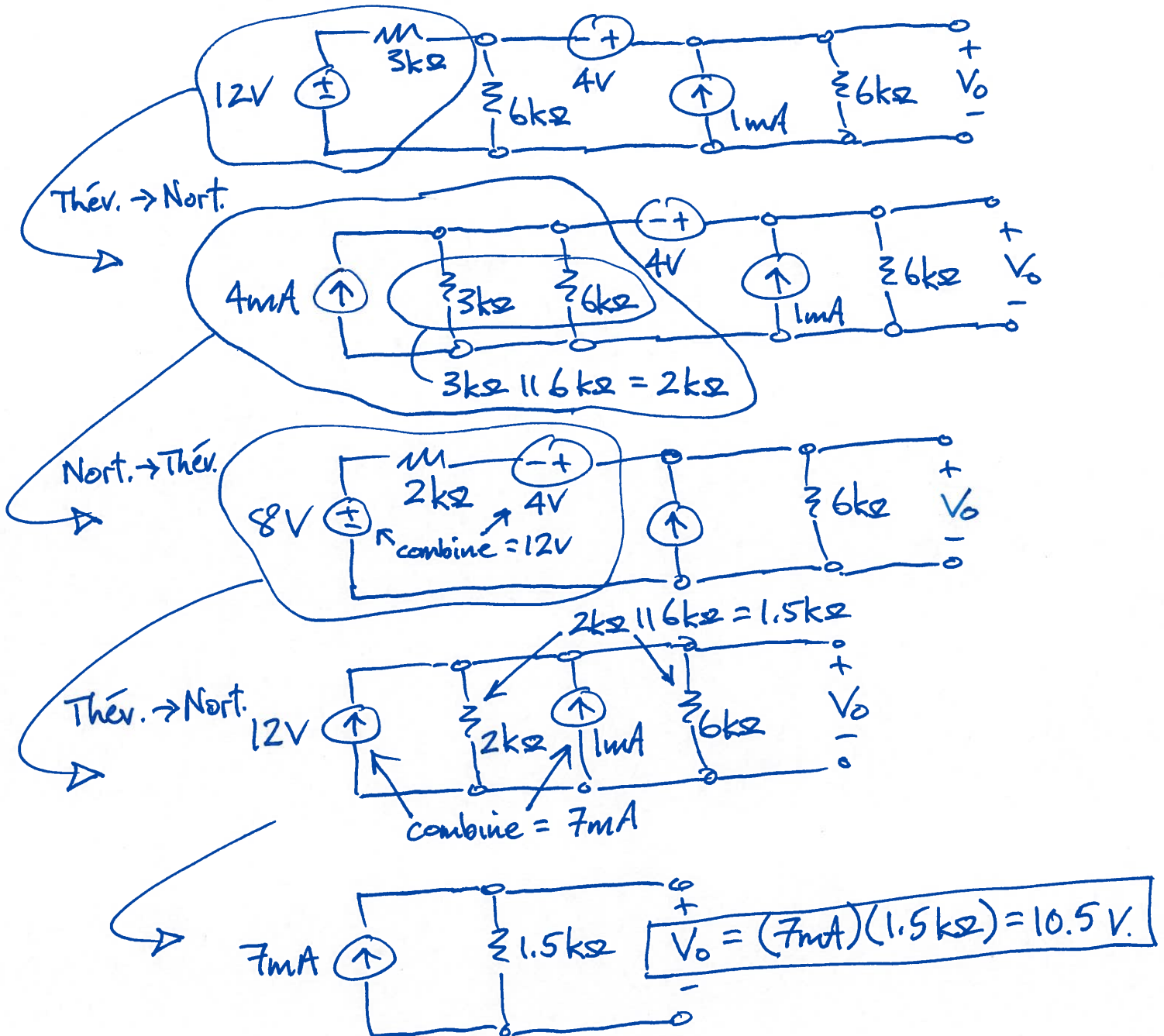(b) (8 marks) Again determine the voltage V_o , but this time use Thévenin's Theorem, Norton's Theorem, or both (i.e., together with one or more source transformations).



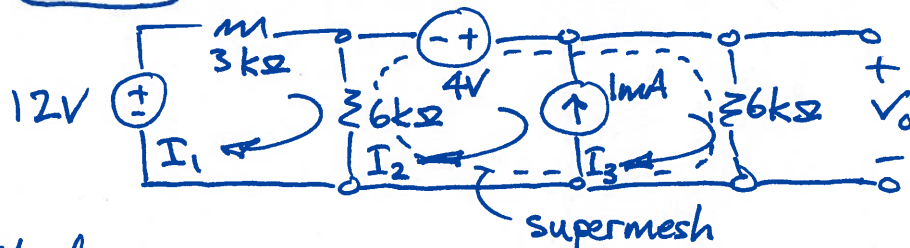(c) (10 marks) Use a loop/mesh analysis to again determine the voltage V_o , as well as the current that flows through the 12-V source.



$$\text{KVL Mesh 1: } -12V + I_1(3k\Omega) + (I_1 - I_2)(6k\Omega) = 0 \quad (1)$$

$$\text{KVL Supermesh: } -4V + I_3(6k\Omega) + (I_2 - I_1)(6k\Omega) = 0 \quad (2)$$

$$\text{Constraint: } I_3 - I_2 = 1mA \quad (3)$$

$$(1) + (3) \rightarrow (2): -4V + (1mA + I_2)(6k\Omega) - 12V + I_1(3k\Omega) = 0$$

$$\hookrightarrow I_2(6k\Omega) + I_1(3k\Omega) = 10V. \quad (4)$$

$$(4) \rightarrow (1): -12V + \left[\frac{10V}{3k\Omega} - \frac{I_2(6k\Omega)}{3k\Omega} \right] (3k\Omega) + \left[\frac{10V}{3k\Omega} - \frac{I_2(6k\Omega)}{3k\Omega} \right] (6k\Omega) - I_2(6k\Omega) = 0$$

$$\hookrightarrow 18V - I_2(6k\Omega + 12k\Omega + 6k\Omega) = 0$$

$$I_2 = \frac{18V}{24k\Omega} = 0.75mA \quad (5)$$

$$(5) \rightarrow (3):$$

$$I_3 = 1mA + 0.75mA = 1.75mA$$

$$\therefore V_o = (6k\Omega)(1.75mA) = 10.5V.$$

$$(5) \rightarrow (4):$$

$$I_1 = \frac{10V - (0.75mA)(6k\Omega)}{3k\Omega}$$

$$= 1.833mA$$

$$= \text{current through 12-V source}$$