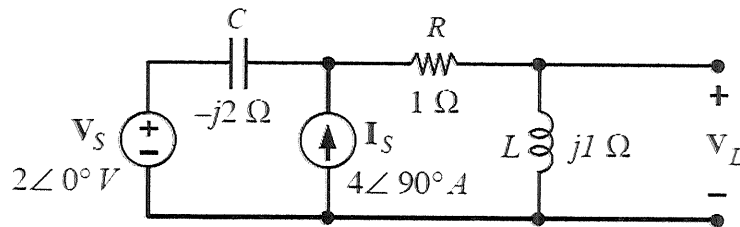


Prob 2. (25 marks)

Consider the circuit shown below which is operating in the (sinusoidal) steady-state at an angular frequency, $\omega = 1000 \text{ rad/s}$.



- (a) [4 marks] Determine the actual component values of the capacitor, C (in farads), and the inductor, L (in henries). Also give the time-domain expressions $v_s(t)$ and $i_s(t)$ for the voltage source and current source, respectively.

$$\omega = 1000 \text{ rad/s}$$


$$Z_C = -j \frac{1}{\omega C} = -j2 \Rightarrow C = 5 \times 10^{-4} \text{ F}$$

$$Z_L = j\omega L = j1 \Rightarrow L = 1 \times 10^{-3} \text{ H}$$

$$V_s = 2\angle 0^\circ \Rightarrow v_s(t) = 2 \cos(1000t) \text{ V}$$

$$I_s = 4\angle 90^\circ \Rightarrow i_s(t) = 4 \cos(1000t + 90^\circ) \text{ A}$$

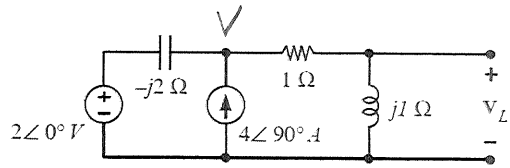(b) [10 marks] Determine the phasor voltage \mathbf{V}_L , across the inductor using *either* Nodal Analysis or Mesh Analysis, and give the corresponding time-domain expression, $v_L(t)$.



Nodal Anal:

$$\text{KCL: } \frac{V - 2\angle 0^\circ}{2\angle -90^\circ} - 4\angle 90^\circ + \frac{V - V_L}{1} = 0$$

$$V_L = V \frac{1\angle 90^\circ}{\sqrt{2}\angle 45^\circ} \rightarrow V = V_L \sqrt{2}\angle -45^\circ$$

$$\frac{V_L \sqrt{2}\angle -45^\circ}{2\angle -90^\circ} - \frac{2\angle 0^\circ}{2\angle -90^\circ} - 4\angle 90^\circ + V_L \sqrt{2}\angle -45^\circ - V_L = 0$$

$$V_L \left(\underbrace{0.707\angle 45^\circ}_{0.5 + j0.5} + \underbrace{\sqrt{2}\angle -45^\circ}_{1 - j1} - 1 \right) = 4\angle 90^\circ + 1\angle 90^\circ$$


$$V_L \left(\underbrace{0.5 - j0.5}_{0.707\angle -45^\circ} \right) = 5\angle 90^\circ$$

$$V_L = \frac{5\angle 90^\circ}{0.707\angle -45^\circ} = 7.07\angle 135^\circ \text{ V.}$$

$$\therefore v_L(t) = 7.07 \cos(1000t + 135^\circ) \text{ V.}$$

This page intentionally left blank as additional workspace.

Mesh Anal:

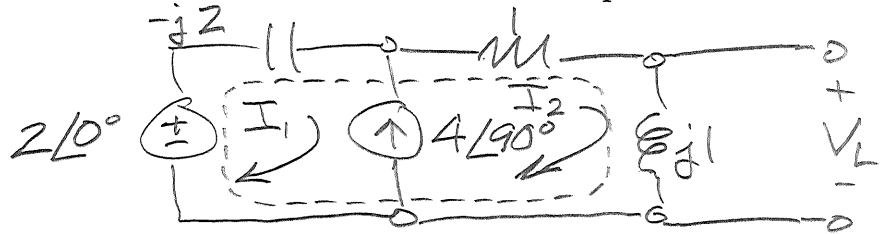

$$\text{KVL: } -2\angle 0^\circ + I_1(2\angle -90^\circ) + I_2(1) + I_2(1\angle 90^\circ) = 0$$

(supermesh) $I_2 - I_1 = 4\angle 90^\circ \rightarrow I_1 = I_2 - 4\angle 90^\circ$

$$I_2(2\angle -90^\circ) - (4\angle 90^\circ)(2\angle -90^\circ) + I_2(1\angle 0^\circ) + I_2(1\angle 90^\circ) = 2\angle 0^\circ$$

$$I_2 \left(\underbrace{2\angle -90^\circ}_{0-j2} + \underbrace{1\angle 0^\circ}_{1+j0} + \underbrace{1\angle 90^\circ}_{0+j1} \right) = \underbrace{2\angle 0^\circ}_{2+j0} + \underbrace{8\angle 0^\circ}_{8+j0}$$


$$I_2(1-j1) = 10+j0$$

$$I_2 = \frac{10\angle 0^\circ}{\sqrt{2}\angle -45^\circ} = 7.07\angle 45^\circ \text{ A.}$$


$$\therefore V_L = (7.07\angle 45^\circ)(1\angle 90^\circ) = 7.07\angle 135^\circ \text{ V.}$$

$$\therefore v_L(t) = 7.07 \cos(1000t + 135^\circ) \text{ V.}$$

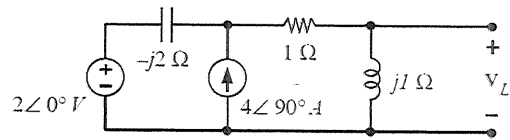(c) [9 marks] Determine the phasor voltage \mathbf{V}_L , across the inductor using Superposition. You do not need to give the corresponding time-domain expression, $v_L(t)$.




V_S alone:

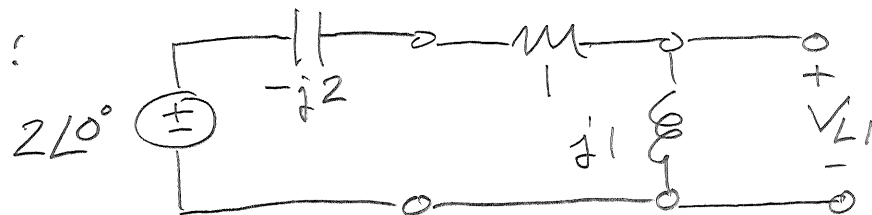

$$V_{L1} = \frac{(2\angle 0^\circ)(1\angle 90^\circ)}{(1 + j1 - j2)} = \frac{(2\angle 0^\circ)(1\angle 90^\circ)}{\sqrt{2}\angle -45^\circ} = 1.414\angle 135^\circ \text{ V.}$$

$$= -1 + j1$$

I_S alone:

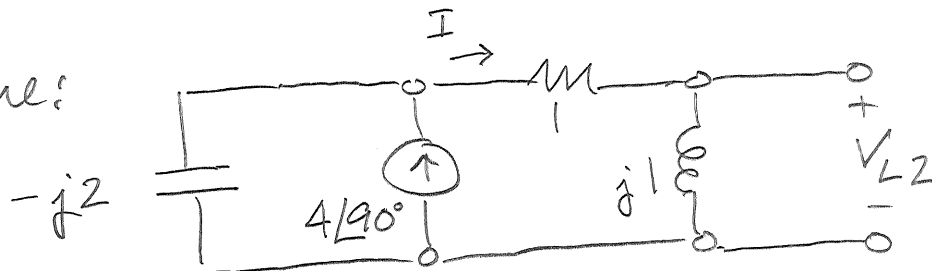

$$I = \frac{(4\angle 90^\circ)(2\angle -90^\circ)}{(1 + j1 - j2)} = \frac{8\angle 0^\circ}{\sqrt{2}\angle -45^\circ} = 5.66\angle 45^\circ \text{ A.}$$


$$V_{L2} = (5.66\angle 45^\circ)(1\angle 90^\circ) = 5.66\angle 135^\circ = -4 + j4 \text{ V}$$

$$V_L = V_{L1} + V_{L2} = (-1 + j1) + (-4 + j4) = -5 + j5 \text{ V.}$$

$$= 7.07\angle 135^\circ \text{ V.}$$

This page intentionally left blank as additional workspace.

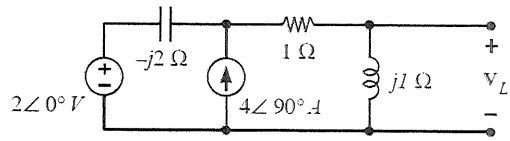(d) [2 marks] If the two sources were not operating at the same frequency, briefly (in 2 or 3 sentences) describe how you would approach the determination of $v_L(t)$.



$v_L(t)$ must be determined by superposition. Here, the phasor component of v_L due to v_S needs to be calc'd using Z values at the freq. of v_S , and the phasor component due to i_S needs to be calc'd using Z values at the freq. of i_S . The 2 phasor components need to be converted to the t -domain separately to yield $v_{L1}(t)$ and $v_{L2}(t)$, since the superposition (sum) must be computed in the t -domain i.e. $v_L(t) = v_{L1}(t) + v_{L2}(t)$.