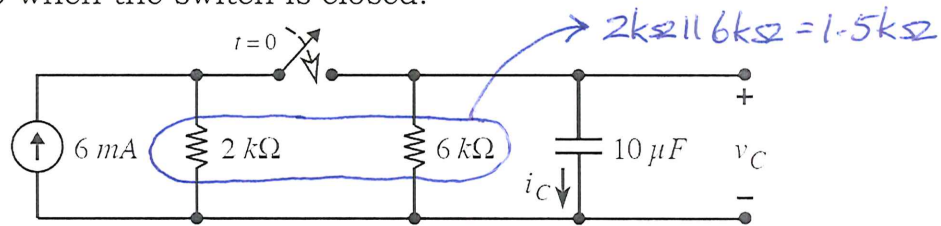


**SA 2. [5 marks]** Consider the following circuit which is in the steady state at  $t = 0$  when the switch is closed.



**(a) [3 marks]** Determine the voltage across the capacitor as a function of time,  $v_C(t)$ , for  $t > 0$ . Assume  $v_C(0) = 0$ .

Recall: 1<sup>st</sup>-order cct. response fctn:  $x(t) = x(\infty) + [x(0+) - x(\infty)]e^{-t/\tau}$

For this case:  $v_C(0) = v_C(0+) = 0$

$$v_C(\infty) = (6\text{mA})(2k\Omega || 6k\Omega) = 9\text{V}$$

$$\tau = R_{TH}C = (2k\Omega || 6k\Omega)(10\mu\text{F}) = 15\text{ms}$$

$$\therefore v_C(t) = 9\text{V} + [0 - 9\text{V}]e^{-t/15\text{ms}}$$

$$\text{or } \boxed{v_C(t) = 9(1 - e^{-t/15\text{ms}})\text{V}}$$

**(b) [2 marks]** Determine the current through the capacitor as a function of time,  $i_C(t)$ , for  $t > 0$ .

Recall: Capacitor Law:  $i_C = C \frac{dv_C}{dt}$

$$\Rightarrow i_C(t) = (10\mu\text{F}) \frac{d}{dt} [9(1 - e^{-t/15\text{ms}})]$$

$$\therefore \boxed{i_C(t) = 6e^{-t/15\text{ms}} \text{ mA}}$$

Alternatively:

$$i_C(0+) = 6\text{mA}$$

$$i_C(\infty) = 0$$

$$\tau = 15\text{ms}$$

$$\therefore i_C(t) = 0 + [6 - 0]e^{-t/\tau}$$

$$\text{or } \boxed{i_C(t) = 6e^{-t/15\text{ms}} \text{ mA}}$$